

Digital logic circuits

Simple circuit

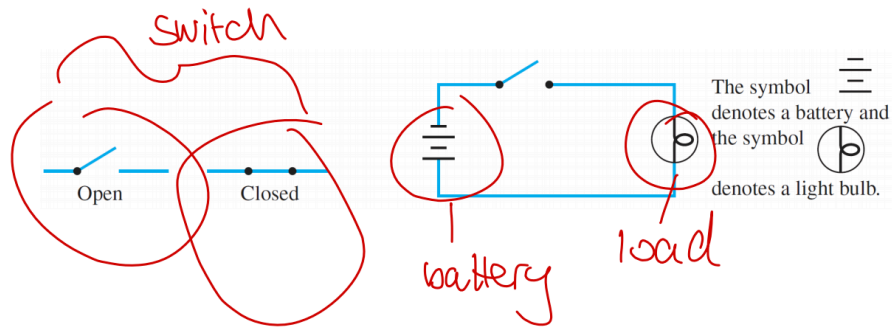


Figure 1: Simple circuit with open and closed switch, battery and load

Combinatorial circuit

Logic gate